

II. Answer *all* questions :

- 13 What are voltage multipliers ?
- 14 Draw the circuit diagram of a choke-input filter circuit.
- 15 What is meant by d.c. loadline ?
- 16 Write De Morgan's theorem.
- 17 Write the relation between α and γ of a common-collector transistor configuration.
- 18 Draw the circuit diagram of an *op-amp* differentiator.
- 19 How negative numbers are represented in binary system ?
- 20 Explain the principle of light emitting diode.
- 21 Write the Boolean expression for X-OR gate.

(9 × 1 = 9 weightage)

III. Answer any *five* questions :

- 22 In a common-base transistor configuration, current gain is 0.9. If the emitter current is 1 mA, calculate the base current.
- 23 A half-wave rectifier uses a diode with $r_p = 300 \Omega$. If the input ac is 200 V (rms) and load is a resistance of 1200Ω , calculate I_{dc} , I_{rms} and rectification efficiency.
- 24 Discuss the method of biasing a transistor with feedback resistor. Explain its advantages.
- 25 Simplify the Boolean expression :
 - (i) $ABC + \overline{ABC} + \overline{ABC} + ABC + \overline{ABC}$.
 - (ii) $(AB + C)(AB + D)$.
- 26 In a transistor CE amplifier, $V_{CC} = 12.5 \text{ V}$, collector load $R_c = 2.5 \text{ k}\Omega$. Draw the DC load line.
- 27 (a) What is meant by amplitude modulation ?
 - (b) An audio signal of 1 kHz is used to modulate a carrier of 500 kHz. Determine the sideband frequencies.
- 28 (a) Define decibel gain. What are the advantages of using decibel units ?
 - (b) Find the gain in dB for a voltage gain of 3D.

(5 × 2 = 10 weightage)

IV. Answer any *two* questions :

- 29 (a) Explain the principle of a Full wave bridge rectifier.
 - (b) Derive the expression for efficiency of the Fullwave Bridge rectifier.
- 30 (a) With a neat circuit diagram, explain the working of a transformer coupled class a amplifier.
 - (b) Discuss its advantages and disadvantages.
- 31 (a) With the help of the truth table, explain the functions of full-adder.
 - (b) Using examples, illustrate the addition of 3-bits by full-adder.

(2 × 4 = 8 weightage)